
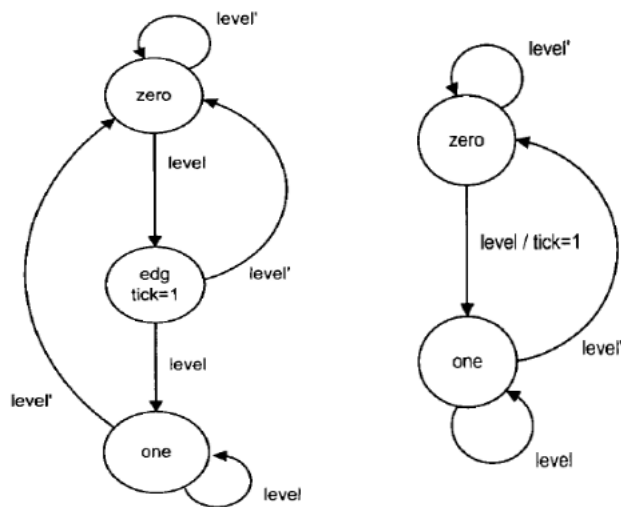


UNIT - 1

 Q1) Write a Verilog code for both the types of Moore and Mealy machines (8M)



Q2) Write HDL code for the given circuit in 2 segment style (10M)



Q3) List out the differences between Asynchronous Reset and Synchronous Reset (7M)

UNIT -2

Q1) With a neat labelled diagram explain about Eye Diagram (9M)

Q2) What are the methods to avoid metastability and with a neat diagram explain about metastability test circuitry (8M)

Q3)

Let's take a practical example of performance increase due to the increase in pipeline stages.

Numbers of pipeline stages were increased from 10 in Pentium III to 20 in Pentium IV resulting in a 20% reduction in instructions per cycle (IPC). Assuming a constant 2% timing overhead as a fraction of the total non-pipelined delay, performance increase is calculated as

(8M)

UNIT – 3

Q1) Explain all the three stages of Equivalence Checking (9M)

Q2) Explain the following: (10M)

- 1) Different Stages of Linting
- 2) Global Routing and Special Routing
- 3) Area capacitance and Fringing capacitance with diagrams
- 4) Different PVT Conditions with diagrams
- 5) Electrical and Logical Effort

Q3) Explain the following: (6M)

- 1) What are the basic standard cells present in a Standard cell library
- 2) Power Planning
- 3) What are the constraints for Synthesis

UNIT – 4

Q1) Explain the following (9M)

- 1) Why is Multi Cycle Path propagation necessary
- 2) MPC Formulation with feedback (with neat diagram)
- 3) Two Flip Flop Synchroniser with neat diagram

Q2)

- **Case – 1 :** $f_A > f_B$ with no idle cycles in both write and read.
- **Transmitter frequency** $f_A = 80\text{MHz}$.
- **Receiver Frequency** $f_B = 50\text{MHz}$.
- Burst Length = No. of data items to be transferred = 120.
- There are no idle cycles in both reading and writing which means that, all the items in the burst will be written and read in consecutive clock cycles.

Case – 3 : $f_A > f_B$ with idle cycles in both write and read.

- Writing frequency = $f_A = 80\text{MHz}$.
- Reading Frequency = $f_B = 50\text{MHz}$.
- Burst Length = No. of data items to be transferred = 120.
- No. of idle cycles between two successive writes is = 1.
- No. of idle cycles between two successive reads is = 3.

(10M)

Q3) Find the minimum delay (6M)

